



BINARY ADDER & BINARY SUBTRACTOR

Jawaher A. Fadhil
Computer science department,
College of science, University of Dohuk

Objectives:

- **1. Half Adder.**
- **2. Full Adder.**
- **3. Binary Adder.**
- **4. Binary Subtractor.**
- **5. Binary Adder-Subtractor.**

1. Half Adder

Half Adder: is a combinational circuit that performs the addition of two bit, this circuit needs two binary inputs and two binary outputs.

Inputs		Outputs	
<i>X</i>	<i>Y</i>	<i>C</i>	<i>S</i>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0
Truth table			



The simplified Boolean function from the truth table:

$$\left\{ \begin{array}{l} S = \bar{X}Y + X\bar{Y} \\ C = XY \end{array} \right. \quad \text{1} \quad \text{(Using sum of product form)}$$

Where *S* is the sum and *C* is the carry.

$$\left\{ \begin{array}{l} S = X \oplus Y \\ C = XY \end{array} \right. \quad \text{2} \quad \text{(Using XOR and AND Gates)}$$

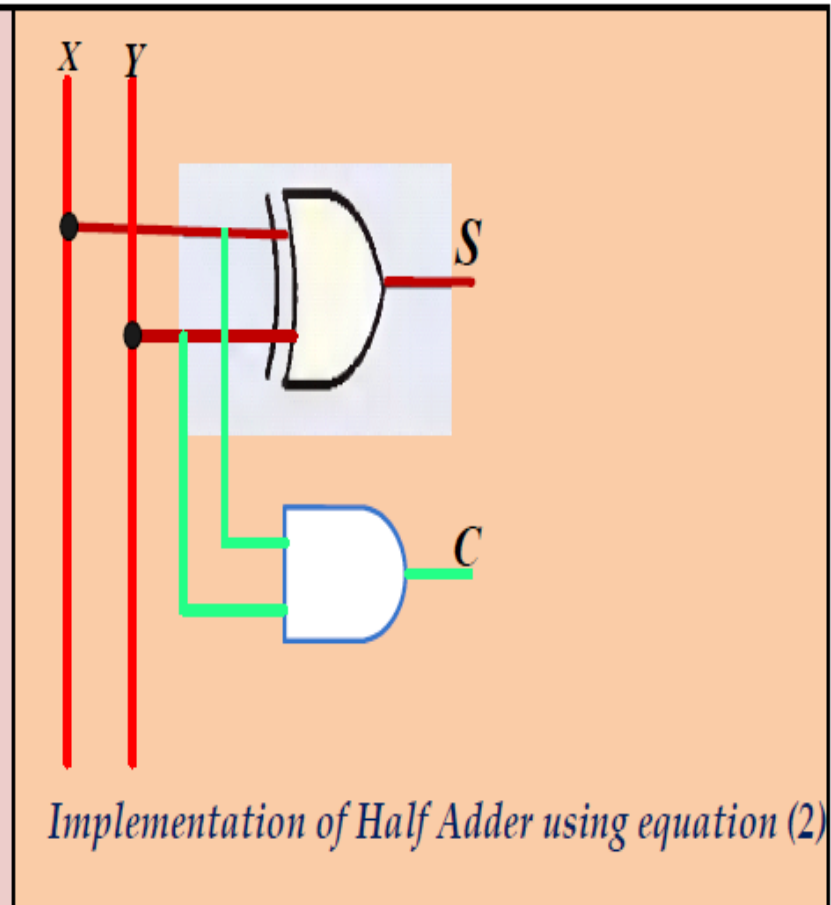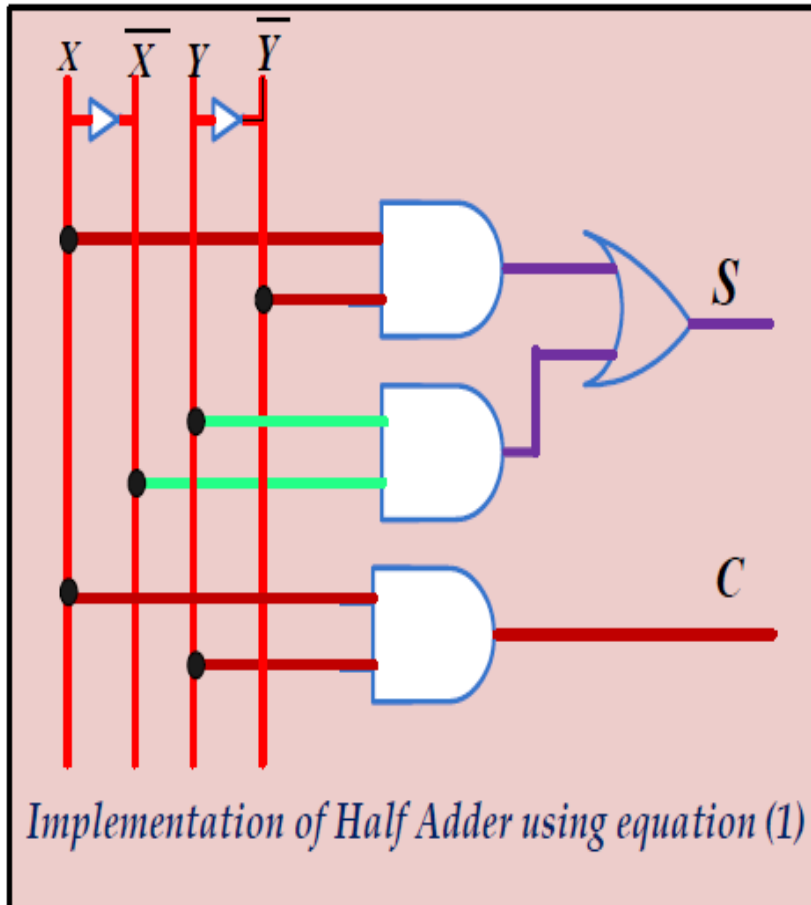- The implementation of half adder using **exclusive-OR** and an **AND** gates is used to show that two half adders can be used to construct a full adder.
- The inputs to the **XOR** gate are also the inputs to the **AND** gate.



2. Full Adder

Full Adder :is a combinational circuit that performs the addition of three bits (two significant bits and previous carry).

- It consists of ***three inputs and two outputs***, two inputs are the bits to be added, the third input represents the carry form the previous position.
- The full adder is usually a component in a cascade of adders, which add 8, 16, etc, binary numbers.

Inputs			Outputs	
X	Y	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Truth table for the full adder

$X \backslash YC_{in}$	00	01	11	10
0	0	1	0	1
1	1	0	1	0


$$S = \overline{X}\overline{Y}C_{in} + \overline{X}Y\overline{C_{in}} + X\overline{Y}\overline{C_{in}} + XYC_{in}$$

$X \backslash YC_{in}$	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C_{out} = XY + XC_{in} + YC_{in}$$

$$\left\{ \begin{array}{l} S = \overline{X}\overline{Y}C_{in} + \overline{X}Y\overline{C_{in}} + X\overline{Y}\overline{C_{in}} + XYC_{in} \\ C_{out} = XY + XC_{in} + YC_{in} \end{array} \right\} \text{ (Sum of products)}$$

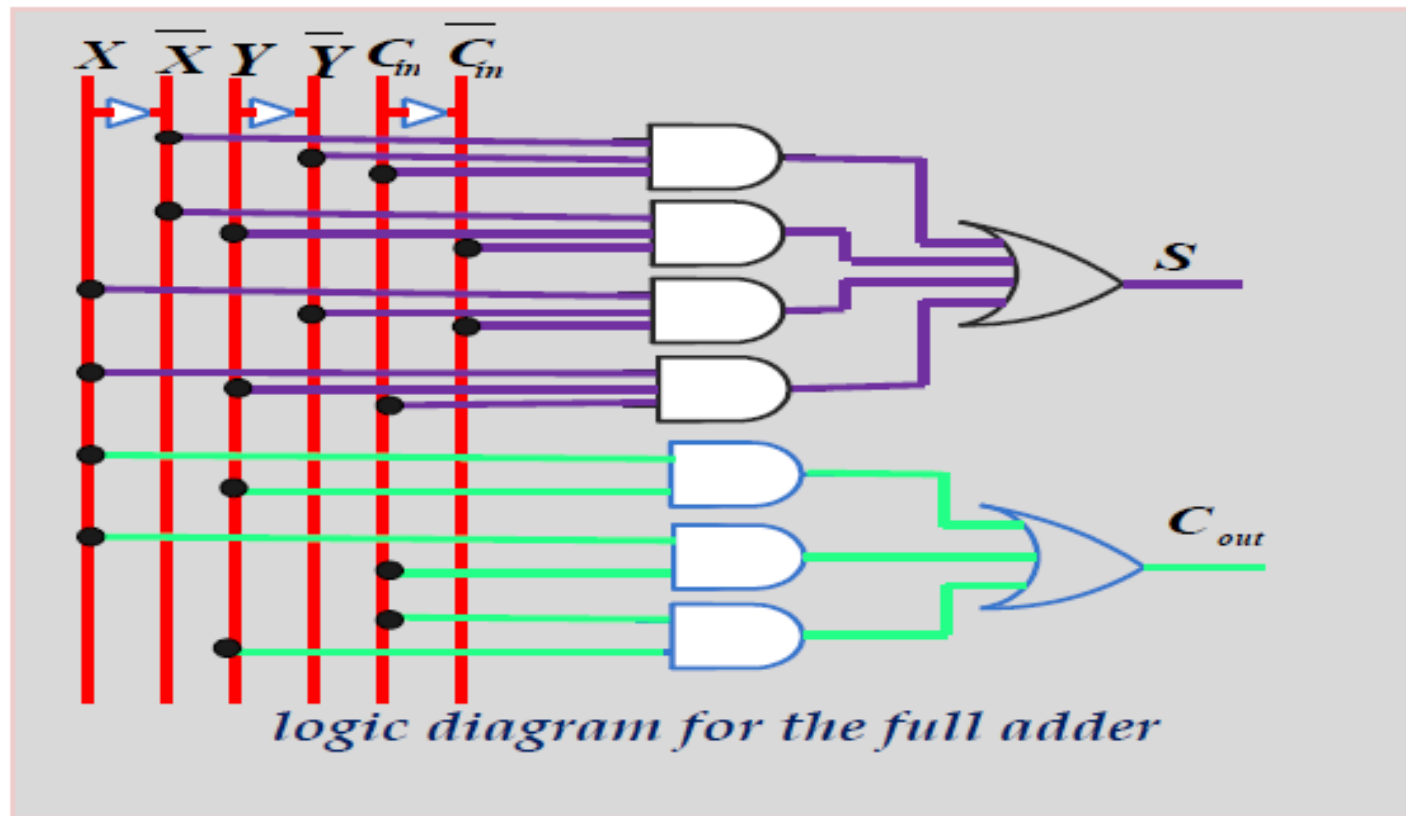
- The *logic diagrams* for the full adder implemented in *sum-of-products* form are the following:



- It can also be implemented using *two half adders* and *one OR gate* (using **XOR** gates).

$$\left\{ \begin{array}{l} S = C_{in} \oplus (X \oplus Y) \\ C_{out} = C_{in} \cdot (X \oplus Y) + XY \end{array} \right\}$$

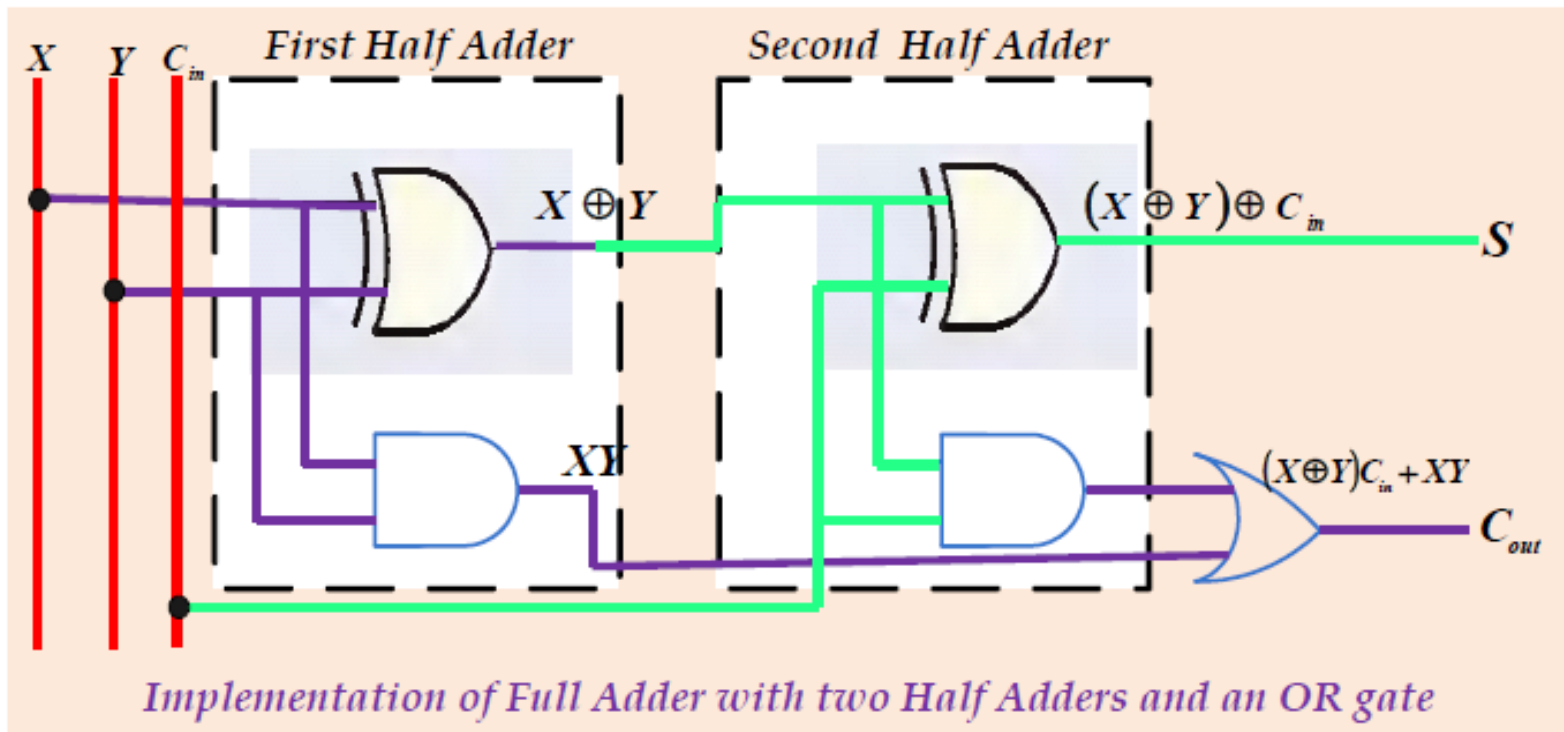
$$\begin{cases} S = C_{in} \oplus (X \oplus Y) \\ C_{out} = C_{in} \cdot (X \oplus Y) + XY \end{cases}$$



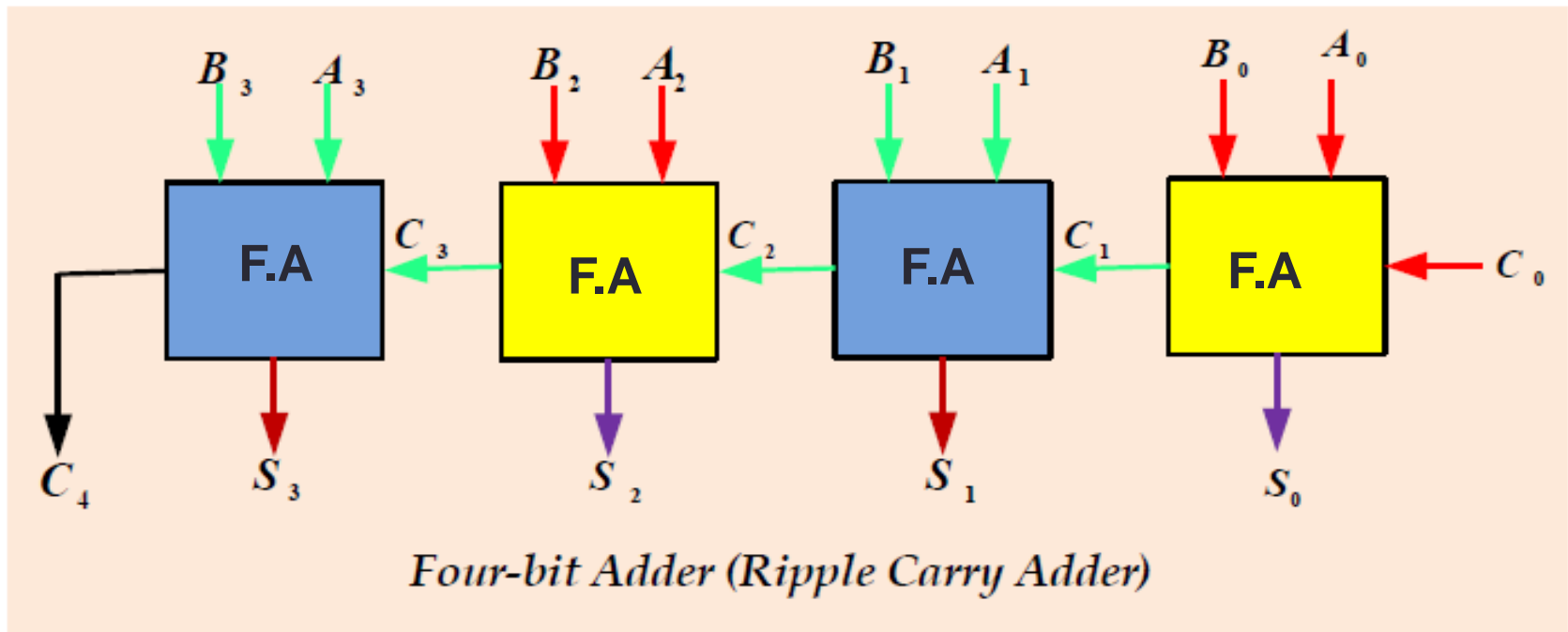3. Binary Adder (Asynchronous Ripple-Carry Adder)

- A binary adder is a digital circuit that produces the ***arithmetic sum of two binary numbers***.
- A binary adder can be constructed with ***full adders connected in cascade*** with the output carry from each full adder connected to the input carry of the next full adder in the chain.
- The ***four-bit adder*** is a typical example of a ***standard component***. It can be used in many applications involving arithmetic operations.

- The input carry to the adder is C_0 and it ripples through the full adders to the output carry C_4 .
- n -bit binary adder requires n full adders.



Example:

$A + B$ ($A = 1011$) and ($B = 0011$)

Subscript i	3	2	1	0	
Input Carry	0	1	1	0	C_i
A	1	0	1	1	A_i
+					
B	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output Carry	0	0	1	1	C_{i+1}

$C_0 = 0$

H.W

- using (**4-bit Ripple-Carry Adder**) Implement the following:

$X + 2Y$ (each one **3-bit**)

$4X + Y$ (x **2-bit** , y **3-bit**)

- Given **a** =111 , **b** =101 , **c** = 1100

Implement $a+b+c$ using full Adder blocks.


4. Binary Subtractor :

- To perform the subtraction $-B$, we can use the **2's complements**, so the subtraction can be converted to addition.
- **2's complement** can be obtained by taking the **1's complement** and adding **1** to the **LSD** bit.
 - 1) **1's complement** can be implemented with invertors.
 - 2) **1** can be added to the sum through the input carry.
- The circuit for subtracting $A - B$ consists of an adder with inverters placed between each data input B and the corresponding input of the full adder.

The input carry C_0 must be equal to 1.

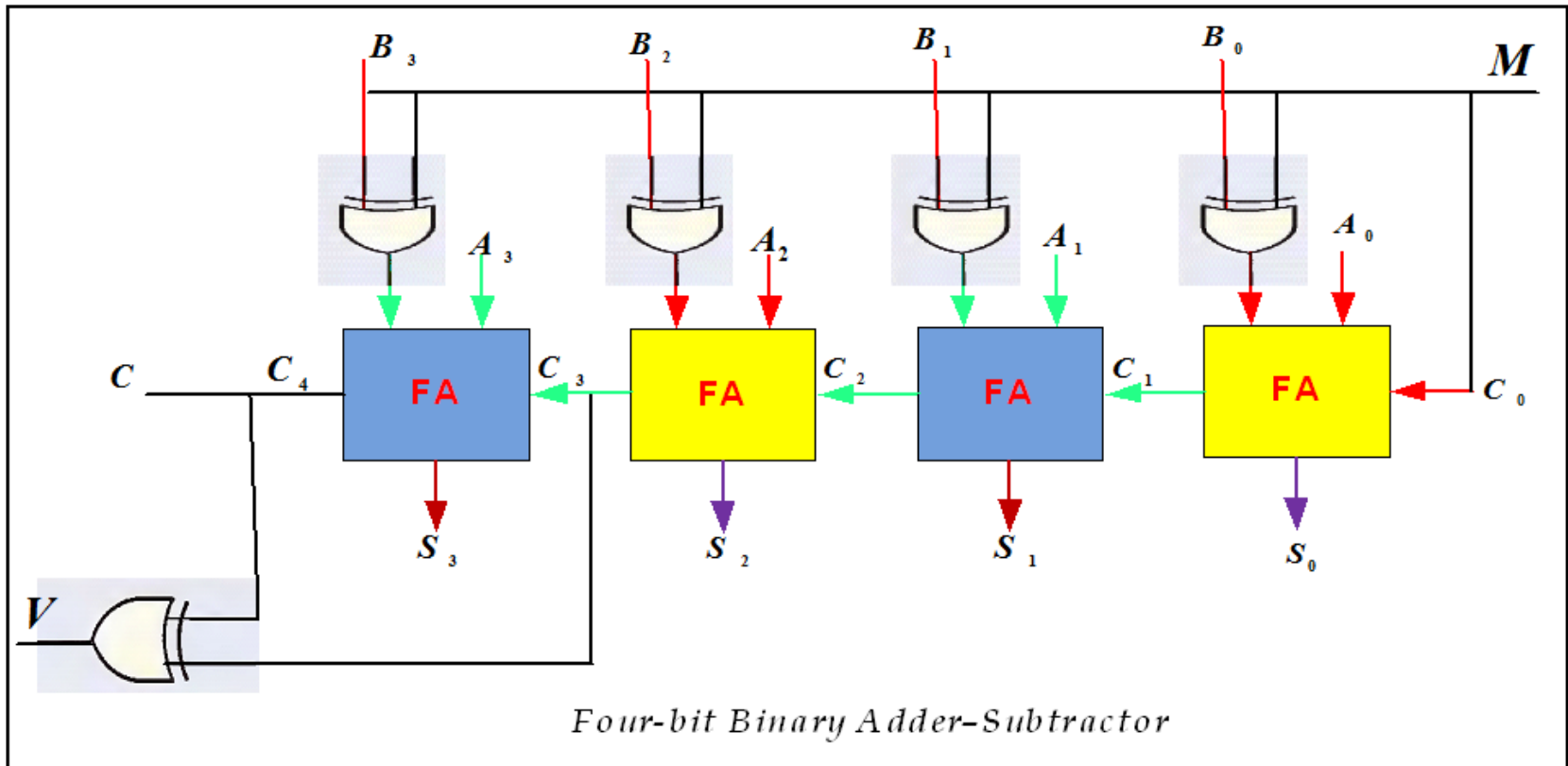5. Binary Adder–Subtractor

- The addition and subtraction operations can be combined into one circuit with one common binary adder by including an *exclusive-OR* gate with each full-adder.



The mode input M controls the operation as the following:

- o $M = 0 \rightarrow$ adder.
- o $M = 1 \rightarrow$ subtractor.
- Each XOR gate receives M signal and B
 - o When $M = 0$ then $B \oplus 0 = B$ and the carry = **0**, then the circuit performs the operation $A + B$.
 - o When $M = 1$ then $B \oplus 1 = \overline{B}$ and the carry = **1**, then the circuit performs the operation $A - B$.
- The *exclusive-OR* with output V is for detecting an overflow.

H.W

- using (4-bit Binary Adder–Subtractor)Implement the following:

$$X + 2Y \text{ (each one 3-bit)}$$

$$4X - Y \text{ (x 2-bit , y 3-bit)}$$

- using (4-bit Binary Adder–Subtractor) Find:
- 9 - 5
 - 15 - 6

*Thank
You*

